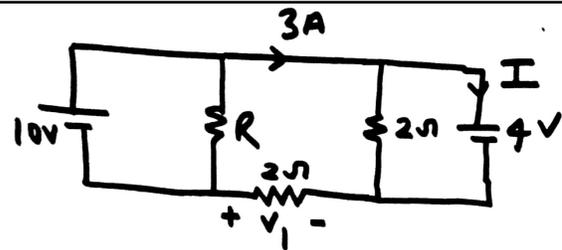


# Linear Circuit Theory


## L05: Concepts of Mutual inductance

- Solution of last lecture question
- Concepts of mutual inductance series parallel connection
- Questions based on mesh analysis

Tutorial problem



$I$  &  $V_1$

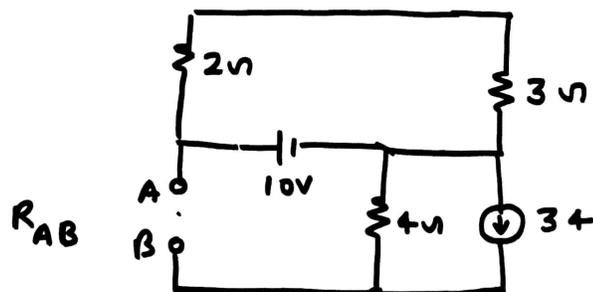

Unknown,  $I_1, I_2, I_3$   
 $V_A, V_B, V_C, V_1$

$$V_A - V_C = 10$$

$$V_B - V_C = 5$$


$$V_A = -V_1 = 2I_2$$

$$V_B = -3V_1$$

$$I_1 + I_2 = -3$$

$$10 + 7I_3 + V_1 = 0$$

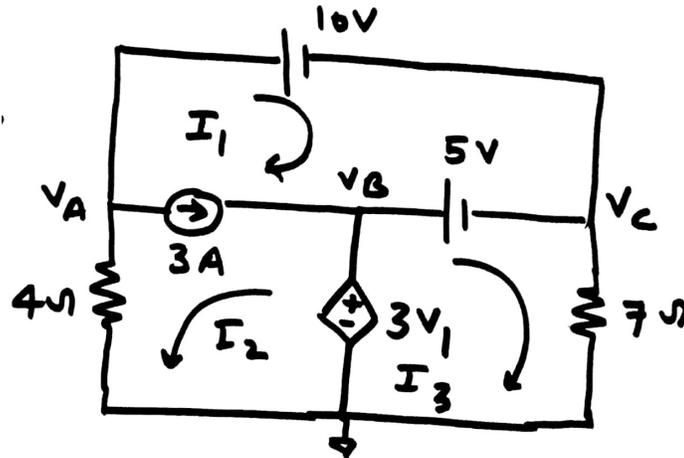Calculate all node voltage  
 and loop current





Concept of mutual inductance

$$V_1 = L_1 \frac{\partial I_1}{\partial t} = L_1 \beta I_1$$

$$V_2 = L_2 \frac{\partial I_2}{\partial t} = L_2 \beta I_1$$

$$M = k \sqrt{L_1 L_2}$$

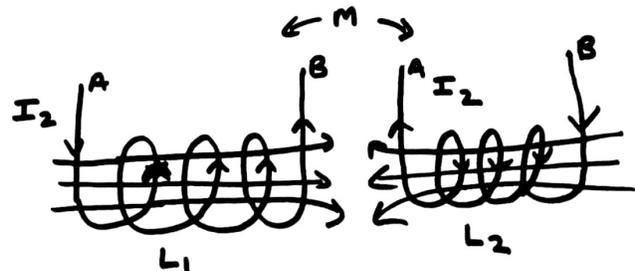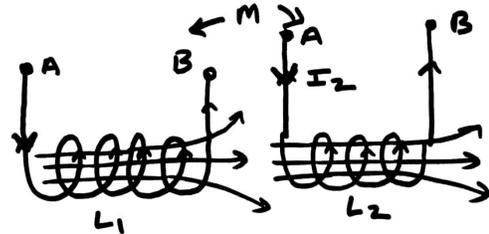

## Voltage current relation in case of coupling

$$V_1 = L_1 \frac{\partial I_1}{\partial t} + M \frac{\partial I_2}{\partial t}$$

~~$$V_1 = L_1 \frac{\partial I_1}{\partial t} + M \frac{\partial I_2}{\partial t}$$~~

$$V_2 = L_2 \frac{\partial I_2}{\partial t} + M \frac{\partial I_1}{\partial t}$$




$$V_1 = L_1 \Delta I_1 + M \Delta I_2$$

$$V_2 = L_2 \Delta I_2 + M \Delta I_1$$

$$V_1 = L_1 \frac{\partial I_1}{\partial t} - M \frac{\partial I_2}{\partial t}$$

$$V_2 = L_2 \frac{\partial I_2}{\partial t} - M \frac{\partial I_1}{\partial t}$$
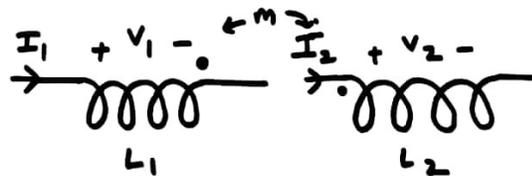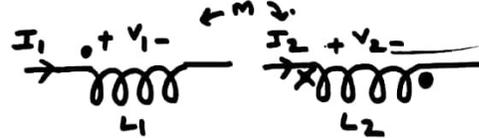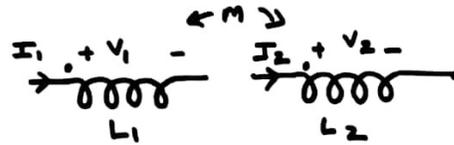
$$V_1 = L_1 \Delta I_1 - M \Delta I_2, \quad V_2 = L_2 \Delta I_2 - M \Delta I_1$$




## Equivalent inductance (Series connection)

$$V = L_1 \frac{\partial I}{\partial t} + L_2 \frac{\partial I}{\partial t} + L_3 \frac{\partial I}{\partial t} +$$

$$2M_{12} \frac{\partial I}{\partial t} - 2M_{23} \frac{\partial I}{\partial t}$$

$$- 2M_{31} \frac{\partial I}{\partial t}$$

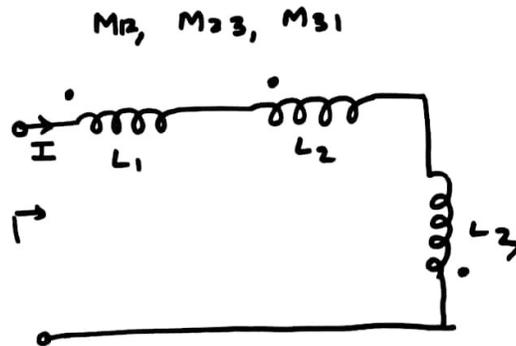
$$L = L_1 + L_2 + L_3 - 2M_{12} - 2M_{23} - 2M_{31}$$


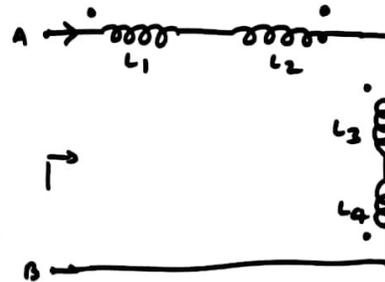
## Problem on Equivalent inductance

$$L_1 = L_2 = L_3 = L_4 = L = 1 \text{ mH}$$

$$M_{12} = M_{23} = M_{31} = M_{41} = M_{24} = M_{34} = 2 \text{ mH}$$



$$L_{\text{eq}} = L_1 + L_2 + L_3 + L_4 +$$

$$- 2M_{12} + 2M_{13} - 2M_{14}$$

$$- 2M_{23} + 2M_{24} - 2M_{34}$$

$$L_{\text{eq}} = 4L - 4M$$

$$L_{\text{eq}} = 4 - 4 \times 2 = -4 \text{ mH}$$

Equivalent inductance in parallel case

$$V = \mu L_{\text{eq}} I$$

$$V = \mu L_1 I_1 + \mu M (I - I_1) \quad -1$$

$$V = \mu L_2 (I - I_1) + \mu M I_1 \quad -2$$

$$\mu L_1 I_1 + \mu M (I - I_1) = \mu L_2 (I - I_1) + \mu M I_1 \quad -3$$

$$I_1 = \frac{I(L_2 - M)}{L_1 + L_2 - 2M} \quad -4$$

$$\text{Eq-1 } V = \mu (L_1 - M) I_1 + \mu M I$$



$$V = \mu \frac{(L_1 - M)(L_2 - M)}{L_1 + L_2 - 2M} I + \mu M I$$

$$L_{\text{eq}} = \frac{L_1 L_2 - M L_2 - M L_1 + M^2}{L_1 + L_2 - 2M} + M$$


$$L_{\text{eq}} = \frac{L_1 L_2 - M^2}{L_1 + L_2 - 2M} \quad , \quad L = \frac{L_1 L_2 - M^2}{L_1 + L_2 + 2M}$$
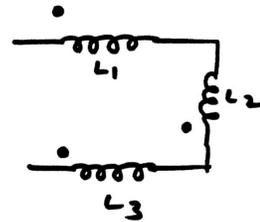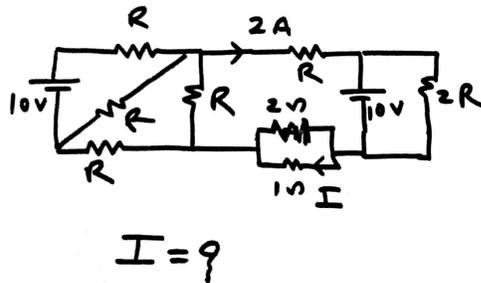
## Numerical Examples

$$\begin{aligned} L_1 &= 1H & M_{12} &= 2H \\ L_2 &= 2H & M_{23} &= 1H \\ L_3 &= 3H & M_{31} &= 1H \end{aligned}$$


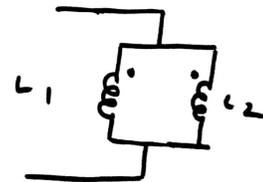
$$\begin{aligned} L_1 &= 1H \\ L_2 &= 3H \\ M_{12} &= 4H \end{aligned}$$



## Next lecture

- Network Theorems (Thevins, Norton's Maximum power transfer)
- Numerical on these theorem

Thank you